


mood-book




UNIT - IV

- ① @ Realization of all gates by NAND Gate
- ② Realization of all gates by NOR Gate


Ans:- @ (i) NOT Gate

 


(ii) AND Gate

 

(iii) OR Gate

 

(iv) Ex-OR Gate

 

$$\begin{aligned}
 Y &= \overline{A \cdot (\overline{A \cdot B}) \cdot B \cdot (\overline{A \cdot B})} \\
 &= \overline{A \cdot (\overline{A \cdot B})} + \overline{B \cdot (\overline{A \cdot B})}
 \end{aligned}$$

$$Y = A \cdot (\overline{A \cdot B}) + B (\overline{A \cdot B})$$


$$= A \cdot (\overline{A} + \overline{B}) + B (\overline{A} + \overline{B})$$

$$= A \cdot \overline{A} + A \cdot \overline{B} + \overline{A} B + B \cdot \overline{B} \quad (\because A \cdot \overline{A} = 0)$$

$$= 0 + A \cdot \overline{B} + \overline{A} B + 0$$

$$Y = A \cdot \overline{B} + \overline{A} B = A \oplus B$$

(V) EX-NOR Gate

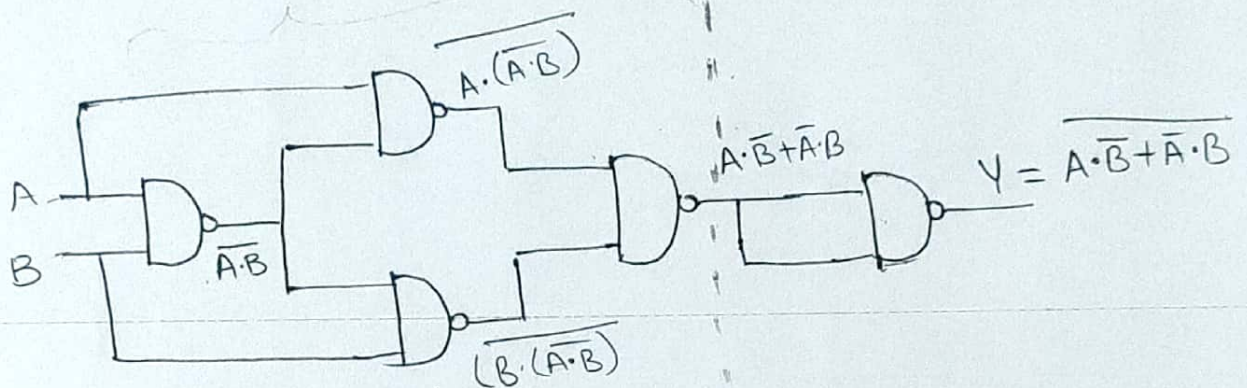

$$Y = \overline{A \cdot B + \overline{A} \cdot B}$$

$$= \overline{(A \cdot B) (\overline{A} \cdot B)}$$


$$= \overline{(\overline{A} + B) (A + B)} = \overline{(\overline{A} + B) (A + B)}$$

$$= \overline{\overline{A} \cdot A + \overline{A} B + AB + B \cdot \overline{B}}$$


$$= \overline{0 + \overline{A} B + AB + B \cdot \overline{B}}$$

$$Y = \overline{\overline{A} B + AB} = \overline{A \oplus B}$$


(vi) NOR Gate

 


(b) (i) NOT Gate

 


(ii) AND Gate

 

(iii) OR Gate

 


(iv) Ex-NOR Gate

 

$$\begin{aligned}
 Y &= A + \overline{A + \bar{B}} + B + \overline{A + \bar{B}} \\
 Y &= \left(\overline{A + \bar{B}} \right) \cdot \left(\overline{B + \bar{A}} \right) \\
 &= \left(A + \overline{A + \bar{B}} \right) \cdot \left(B + \overline{A + \bar{B}} \right) \\
 &= \left(A + (\bar{A} \cdot \bar{B}) \right) \cdot \left(B + \bar{A} \cdot \bar{B} \right)
 \end{aligned}$$


$$\begin{aligned}
 &= (A+\bar{A}) (A+\bar{B}) \cdot (B+\bar{A}) \cdot (B+\bar{B}) \quad \because (A+\bar{A} = 1) \\
 &= 1 (A+\bar{B}) \cdot (B+\bar{A}) \cdot 1 \\
 &= (A+\bar{B}) (B+\bar{A}) \\
 &= AB + A\bar{A} + B\bar{B} + \bar{A}\bar{B} \\
 &= AB + 0 + 0 + \bar{A}\bar{B} \\
 Y &= AB + \bar{A}\bar{B} = \overline{A \oplus B}
 \end{aligned}$$

(V) EX-NOR Gate:

 

$$\begin{aligned}
 Y &= \overline{AB + \bar{A}\bar{B}} \\
 &= (\overline{AB}) (\overline{\bar{A}\bar{B}}) \\
 &= (\bar{A} + \bar{B}) (\overline{\bar{A} + \bar{B}}) \\
 &= (\bar{A} + \bar{B}) (A + B) \\
 &= \bar{A} \cdot A + \bar{A}B + A\bar{B} + B \cdot \bar{B} \\
 &= 0 + \bar{A}B + A\bar{B} + 0 \\
 Y &= \bar{A}B + A\bar{B} = A \oplus B
 \end{aligned}$$

(vi) NAND Gate:

 

② Explain and design the logic diagram of a circuit for 4 bit parallel Adder / Subtractor?

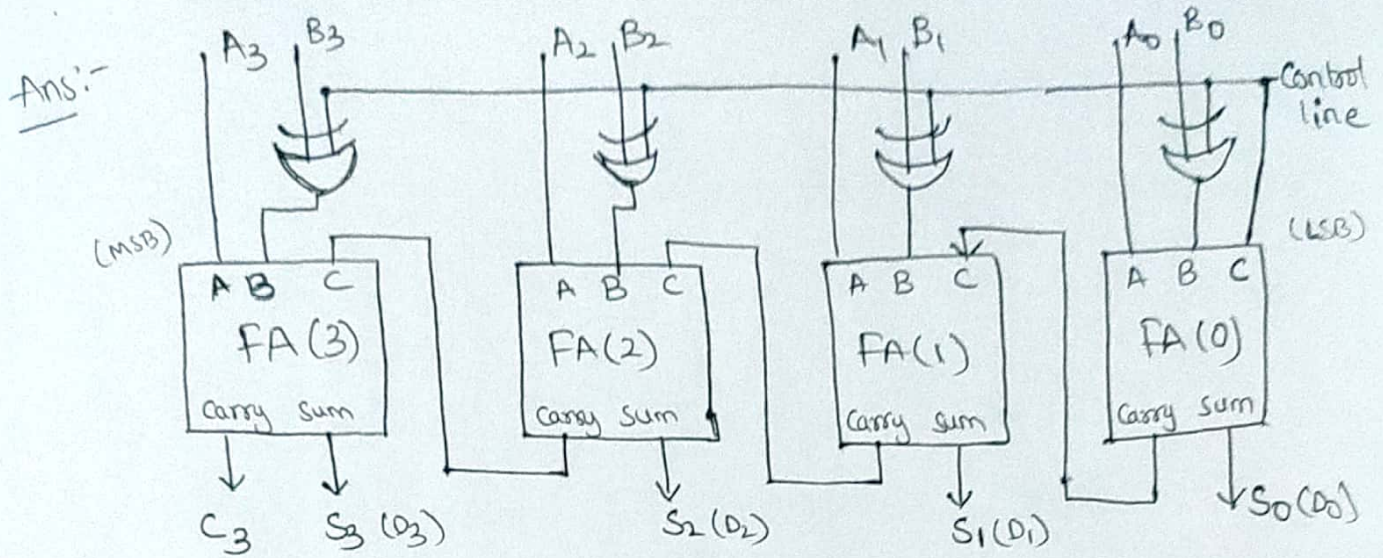


fig: 4 bit parallel adder / Subtractor.

→ The 4 bit parallel binary adder / Subtractor circuit is shown in above figure.

→ To perform the operation of both ^{4 bit} addition and subtraction. It required 4 full adders (FA). Each full adder has three inputs (i.e., A, B & C) and two outputs (i.e., Sum and Carry).

→ For 4 bit parallel adder / Subtractor, it has two 4 bit inputs $A_3 A_2 A_1 A_0$ and $B_3 B_2 B_1 B_0$. The control line, connected with C of the least significant bit (LSB) of the full adder, is used to perform the operations of addition and subtraction.

→ The Ex-OR gates are used as controlled inverters.

→ In a computer, one has to carry out the addition as well as subtraction. Hence it is more convenient to have a single circuit out both these arithmetic functions instead of two different circuits.

→ The binary subtraction can be converted into the addition by considering the 2's complement method.

→ In the circuit, when control line = 0, the circuit acts as an adder; the number $B_3 B_2 B_1 B_0$ is added to $A_3 A_2 A_1 A_0$ and gives $\text{Sum} = S_3 S_2 S_1 S_0$.

When control line = 1, the circuit acts as subtractor, the number $B_3 B_2 B_1 B_0$ is subtracted from $A_3 A_2 A_1 A_0$ and gives the ~~D~~ifference = $D_3 D_2 D_1 D_0$.

Operation:

- (1) Adder :- When control line = 0, the output of the Ex-OR gates will be same as the B data bits. The carry input to the first full adder is 0 (ie., control line = 0). Hence A and B bits are applied as the two inputs to the parallel adder. Thus the output would correspond to the sum of A & B.


② Subtractor: when control line = 1, then the output of the EX-OR gates will be the complement of the ~~B data bits~~ B data bits. The carry input to the first full adder is now 1 (ie, control line = 1). Hence addition of 1 to the 1's complement of B bits forms the 2's complement B bits are applied as the inputs to the parallel adder. This is the process of subtracting a binary number from another using 2's complement method.

③ Implement the logic function $F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9)$ using (i) 16:1 MUX (ii) 8:1 MUX (iii) 4:1 MUX

Ans (i) 16:1 MUX

$$16 = 2^4$$

 
for 16:1 MUX, it has 16 inputs, ~~and~~ one output & 4 select lines.



(ii) 8:1 MUX

BCD \rightarrow inputs are used for selection lines i.e.

	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	1	0	\bar{A}	\bar{A}	0	0	A

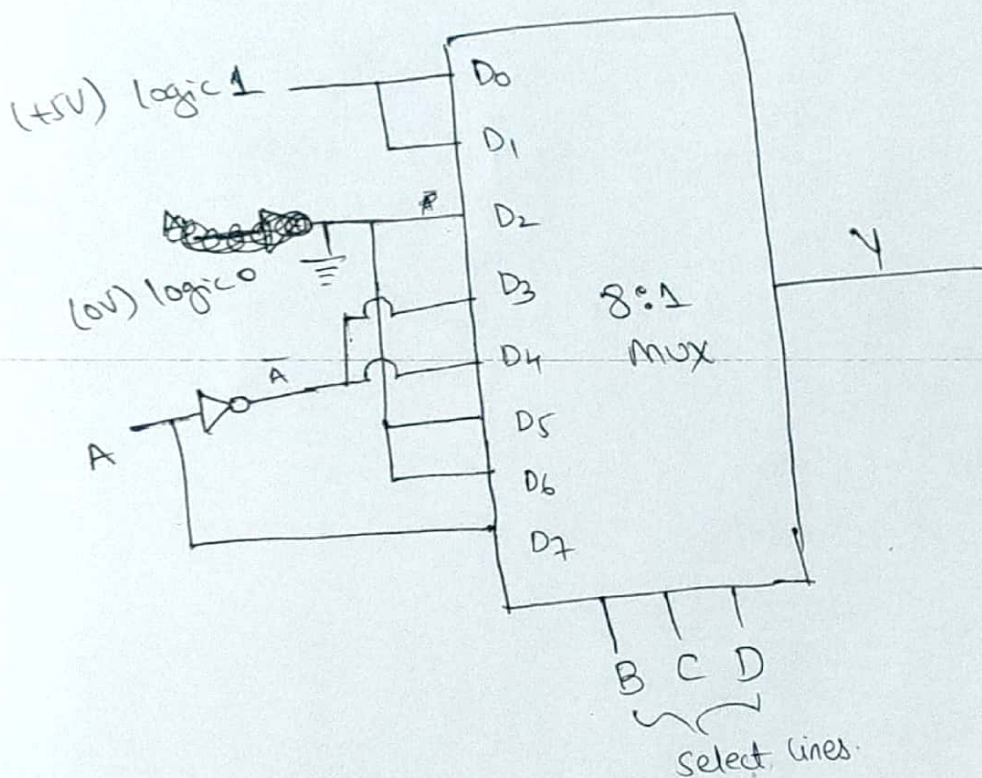

(iii) 4:1 MUX

CD \rightarrow inputs are used for select lines.

	D_0	D_1	D_2	D_3
$\bar{A}\bar{B}$	0	1	2	3
$A\bar{B}$	4	5	6	7
$\bar{A}B$	8	9	10	11
AB	12	13	14	15
	F_1	F_2	$F_3=0$	F_4

$$\begin{aligned}
 F_1 &= \overline{A}B + A\overline{B} + \overline{A}B \\
 &= \overline{A}(B+B) + A\overline{B} \\
 &= \overline{A} + A\overline{B} \\
 &= (\overline{A}+A)(\overline{A}+\overline{B})
 \end{aligned}$$

$$\Rightarrow \boxed{F_1 = \overline{A} + \overline{B}} \equiv D_0$$


$$\begin{aligned}
 F_2 &= \overline{A}\overline{B} + \overline{A}B \\
 &= \overline{A}(\overline{B}+B)
 \end{aligned}$$

$$\Rightarrow \boxed{F_2 = \overline{A}} \equiv D_1$$

$$\Rightarrow \boxed{F_3 = 0} \equiv D_2$$

$$F_4 = \overline{A}\overline{B} + AB$$
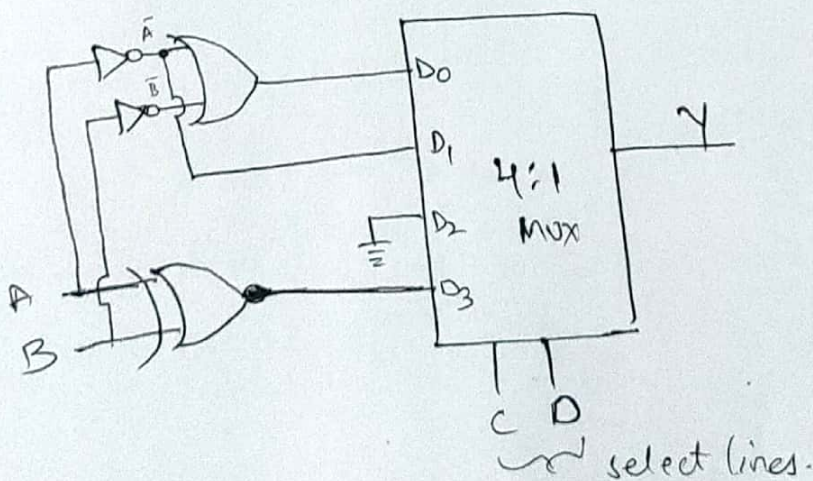
$$\Rightarrow \boxed{F_4 = A \oplus B} \equiv D_3$$



4) Explain the working of 2 bit comparator.

Ans:- Comparator:-

A Comparator is a logic circuit that compares the value of two numbers. Let us assume that the bits A & B are compared. The truth table for the Comparator action as shown below.

Inputs		Outputs		
A	B	A > B	A = B	A < B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

Truth table for one bit Comparator.


From the truth table, the Expression for the outputs $A > B$, $A = B$ and $A < B$ can be written as

$$A > B \Rightarrow A \cdot \bar{B}$$

$$A = B \Rightarrow \overline{A \oplus B}$$

$$A < B \Rightarrow \bar{A} \cdot B$$

 The single bit comparator can be realized by using logic gates,



Two bit Comparator :-

Let the numbers to be compared be $A (A_1, A_0)$
and $B (B_1, B_0)$.

→ A will be greater than B when any one of the following conditions is satisfied.

- ① when $A_1 = 1, B_1 = 0$ irrespective of other bits
- ② If $A_1 = B_1$ and $A_0 = 1, B_0 = 0$.

→ A will be Equal to B when the following conditions satisfied.

- ① $A_1 = B_1, A_0 = B_0$.

→ A will be less than B when any one of the following conditions is satisfied.

- ① when $A_1 = 0, B_1 = 1$ irrespective of other bits
- ② If $A_1 = B_1$ and $A_0 = 0, B_0 = 1$

→ To represent these conditions in the form of a truth table, ^{it} requires 16 combinations & hence a function table is given as.

Inputs		Outputs		
$A_1 \& B_1$	$A_0 \& B_0$	$A > B$	$A = B$	$A < B$
$A_1 > B_1$	X	1	0	0
$A_1 < B_1$	X	0	0	1
$A_1 = B_1$	$A_0 > B_0$	1	0	0
$A_1 = B_1$	$A_0 < B_0$	0	0	1
$A_1 = B_1$	$A_0 = B_0$	0	1	0

Function table of 2 bit Comparator.


→ In the function table, a X indicates the don't care condition. From the function table, the Expressions for $A > B$, $A = B$ & $A < B$.

$$A > B \Rightarrow A_1 \bar{B}_1 + \overline{A_1 \oplus B_1} \cdot A_0 \bar{B}_0$$

$$A = B \Rightarrow \overline{A_1 \oplus B_1} \cdot \overline{A_0 \oplus B_0}$$

$$A < B \Rightarrow \bar{A}_1 B_1 + \overline{A_1 \oplus B_1} \cdot \bar{A}_0 B_0$$

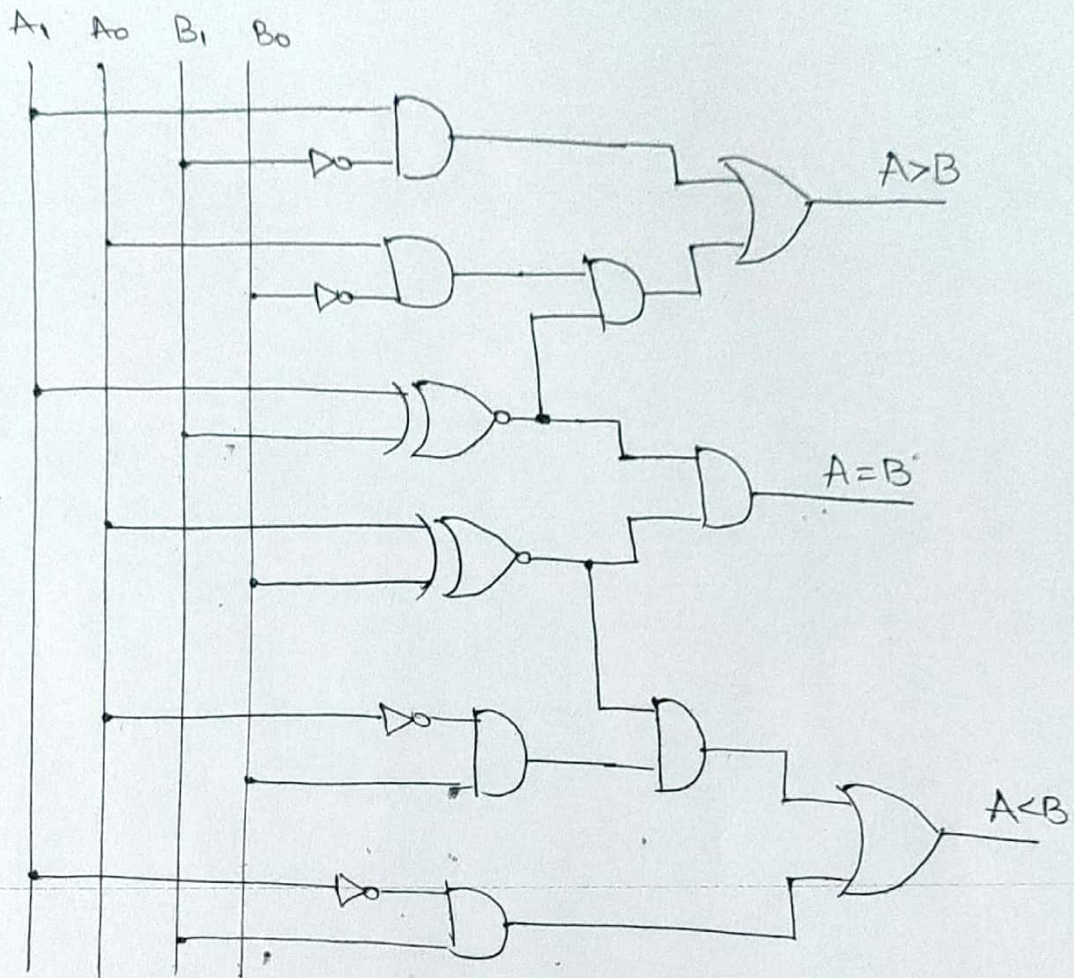→ The two bit Comparator can be realized by using logic gates,




⑤ Explain about Encoders and Decoders with Suitable Examples?

Ans:- Encoders:

- The Encoder circuit is used to convert one form of data into binary form.
- The input of data may be in form other than binary i.e. decimal, octal, hexadecimal etc.
- Encoders are required at the interface of man-machine communication and for transmission of data between the various digital subsystems that do not employ the same code.

→ The Encoders can also be designed using combinational logic circuits.

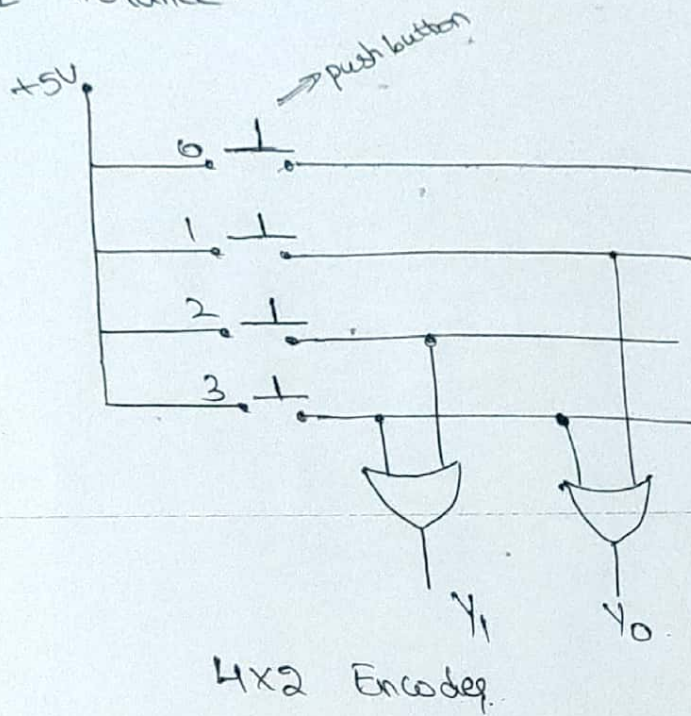→ The circuit diagram of 4x2 Encoder, this circuit converts decimal numbers 0, 1, 2 and 3 into binary for instance.



position of the push button (Input)	Outputs	
	Y_1	Y_0
0	0	0
1	0	1
2	1	0
3	1	1

Table of 4x2 Encoder

→ When push button 0 is pressed, the Y_1 and Y_0 OR gates have low outputs, therefore output word is $Y_1 Y_0 = 00$.

→ If the button 1 is keyed, the Y_1 and Y_0 OR gates have low and high outputs, therefore the output word is $Y_1 Y_0 = 01$.


→ Similarly when the button 2 is keyed the output word is $Y_1 Y_0 = 10$.

→ When the button 3 is keyed the output word is $Y_1 Y_0 = 11$.

Decimal to binary Encoder:-

position of the push button (input)	outputs			
	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

Table of Decimal to binary Encoder.

 

Decimal to binary Encoder

Decoders:

- The decoder is the opposite of the Encoder.
- This circuit converts binary data in to other form i.e., decimal, octal, hexadecimal etc.
- Decoder is a Combinational logic circuit which accepts the states from various inputs and delivers a logic 1 at any one of the 2^n outputs.
- Thus the decoder circuits of 2 input lines gives $2^2 = 4$ outputs, similarly the 3 input decoder gives $2^3 = 8$ outputs.

2x4 Decoder: [2 inputs, 4 outputs]

- When the inputs A & B are 0 then the output of Y_0 AND gate is 1 because all inputs of the Y_0 gate is high & outputs of other AND gates are low, because atleast one input is low for these.
- for inputs $A=0$ & $B=1$, then $Y_1=1$.
- for inputs $A=1$ & $B=0$, then $Y_2=1$
- for inputs $A=1$ & $B=1$, then $Y_3=1$
- Therefore in an decoder only one output is high for one combination and other outputs low.

Inputs		Outputs			
A	B	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Table of 2x4 Decoder

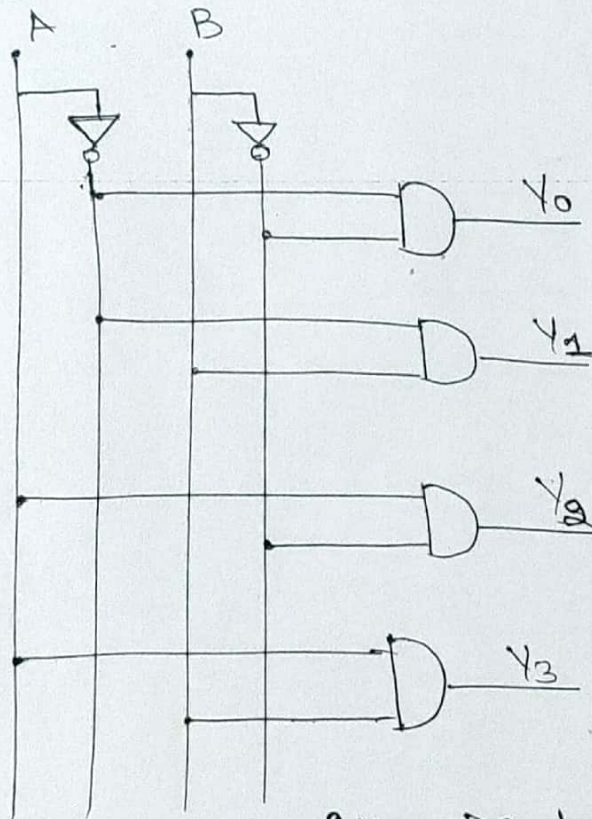


fig: 2x4 Decoder.

3x8 Decoder:

→ For instance when $A=0$, $B=0$ & $C=0$, the Y_0 AND gate has all high inputs, therefore the Y_0 is high. Furthermore, all other AND gates have at least one low input as a result all other AND gates have low outputs.

Inputs			Outputs							
A	B	C	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Table of 3x8 Decoder.

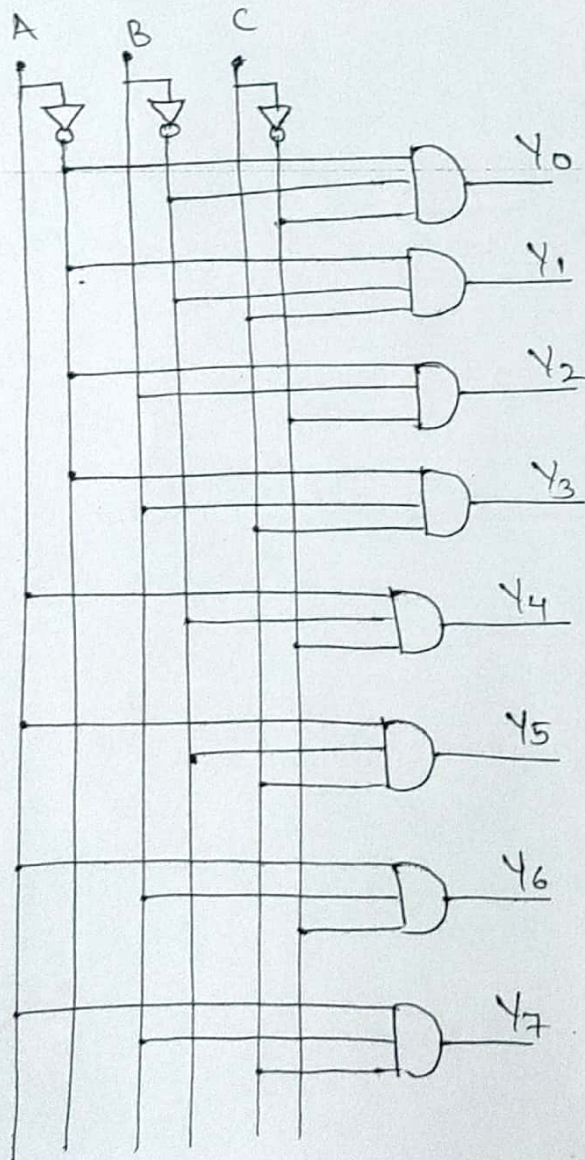



Fig: 3x8 decoder.

⑥ @ Simplify the following function using k-map method
 $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 6, 9, 10) + d(7, 11, 12, 13, 15)$

⑦ Simplify the following function using k-map method
 obtain (i) minimal SOP & (ii) minimal POS Expression.

$F(x, y, z) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$

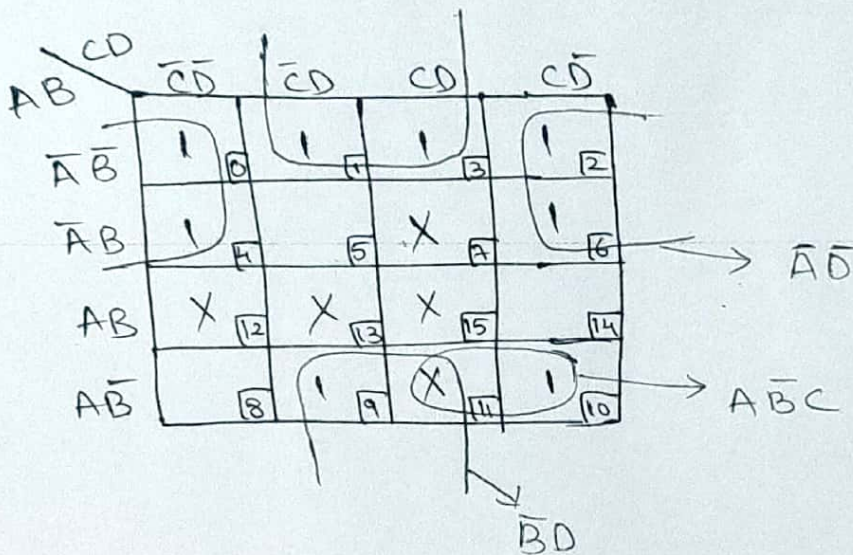
Ans: @ $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 6, 9, 10) + d(7, 11, 12, 13, 15)$



$F(A, B, C, D) = \bar{A}\bar{D} + A\bar{B}C + \bar{B}D.$

⑦ (i) minimal SOP.

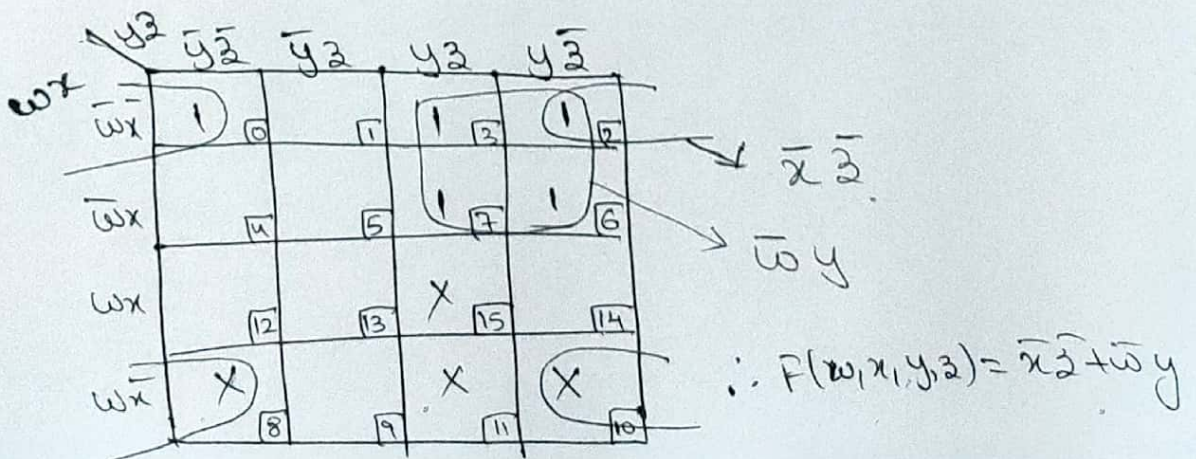$F(x, y, z) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$




$\therefore F(w, x, y, z) = \bar{x}\bar{z} + \bar{w}y$

(ii) Minimal POS Expression: (20)

$$\text{given } F(w, x, y, z) = \Sigma(0, 2, 3, 6, 7) + d(8, 10, 11, 15)$$

$$\text{pos } \overline{F}(w, x, y, z) = \Pi(1, 4, 5, 9, 12, 13, 14) + d(8, 10, 11, 15)$$

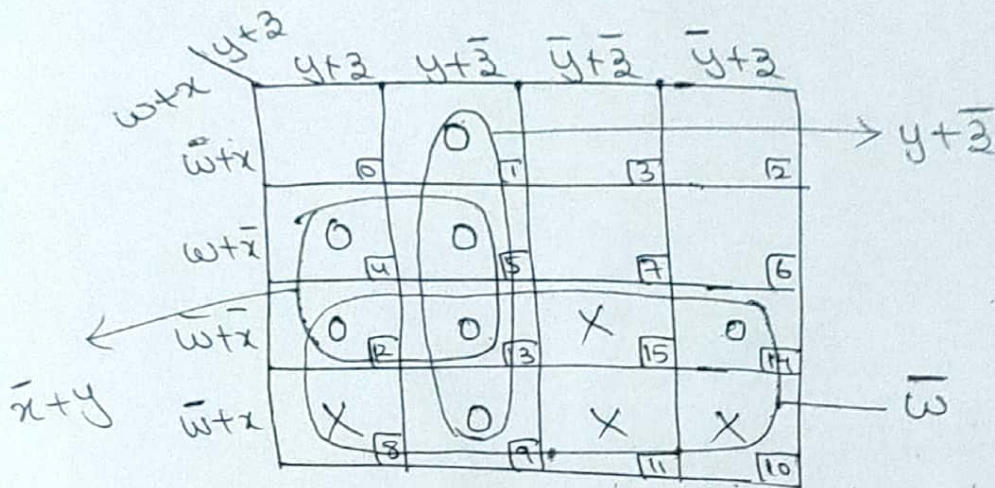minimal POS

$$F(w, x, y, z) = (\overline{w})(y+\overline{z})(\overline{x}+y)$$

Short Answers:-

- (i) (a) List the properties of boolean Algebra?
- (b) State Duality & Demorgan's theorem?

Ans:- (a) properties of Boolean Algebra:-

→ Boolean algebra is a mathematical system consisting of a set of two (or) more distinct elements, "two binary" operators denoted by the symbols (+) & (·) and one "unary" operator denoted by the symbol either bar (-) or prime (').

① Commutative property:

$$A+B = B+A$$

$$A \cdot B = B \cdot A$$

② Associative property:

$$A+(B+C) = (A+B)+C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

③ Distributive property:

$$A+BC = (A+B)(A+C)$$

$$A \cdot (B+C) = (A \cdot B) + (A \cdot C)$$

④ Complementary property:

$$A+\bar{A} = 1$$

$$A \cdot \bar{A} = 0$$

⑤ Involution property:-

$$(A')' = A \quad (\text{or}) \quad \overline{\bar{A}} = A$$

⑥ Idempotency property:-

$$A+A = A$$

$$A \cdot A = A$$

⑦ Absorption Law:

$$A+\bar{A}B = A+B$$

⑧ Consensus law:

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

↳ This law is used to eliminate redundant term from the boolean expression.

⑥ Duality Theorem:-

The duality of the function can be obtained by interchanging OR (+) \leftrightarrow AND (.) $\&$ AND (.) \leftrightarrow OR (+)

ex:- ① $y = x + y$

$$y_d \text{ (duality function)} = x \cdot y$$

② $F = \bar{A}B + CD$

$$F_d = (\bar{A} + B) \cdot (C + D)$$

DeMorgan's Theorem:-

→ DeMorgan's 1st Theorem:

It stated as, the complement of a product of variables is equal to the sum of ^{individual} complement of the variables

$$\overline{AB} = \bar{A} + \bar{B}$$

A	B	\overline{AB}	$\bar{A} + \bar{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

→ De Morgan's 2nd Theorem:-

It stated as, the Complement of a sum of variables is equal to the product of individual complement of the variables

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

AB	$\overline{A+B}$	$\bar{A} \cdot \bar{B}$
0 0	1	1
0 1	0	0
1 0	0	0
1 1	0	0

(2) (a) Simply the given Expression

$$Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC$$

(b) Find the Complement of the Expression

$$Y = ABC + A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C$$

Ans: (a) $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + ABC$

$$= \bar{B}\bar{C}(\bar{A}+A) + A\bar{B}C + AB(C+\bar{C})$$

$$= \bar{B}\bar{C} \cdot 1 + \bar{A}BC + AB \cdot 1$$

$$= \bar{B}\bar{C} + \bar{A}BC + AB$$

$$= \bar{B}(\bar{C} + \bar{A}C) + AB$$

$$= \bar{B}((\bar{C} + \bar{A})(\bar{C} + C)) + AB$$

$$= \bar{B}((\bar{C} + \bar{A}) \cdot 1) + AB$$

$$= \bar{B}(\bar{C} + \bar{A}) + AB$$

$$= \bar{B}\bar{C} + \bar{A}\bar{B} + AB$$

$$= \bar{B}\bar{C} + A(B + \bar{B})$$

$$Y = A + \bar{B}\bar{C} //$$

$$\textcircled{b} \quad Y = ABC + AB\bar{C} + \bar{A}\bar{B}C + \bar{A}BC$$

$$\bar{Y} = \overline{ABC + AB\bar{C} + \bar{A}\bar{B}C + \bar{A}BC}$$

$$= \overline{AB(C + \bar{C}) + \bar{A}C(\bar{B} + B)}$$

$$= \overline{AB \cdot 1 + \bar{A}C \cdot 1}$$

$$= \overline{AB + \bar{A}C}$$


$$= (\overline{AB}) (\overline{\bar{A}C})$$

$$\bar{Y} = (\bar{A} + \bar{B}) (A + \bar{C}) //$$

$\textcircled{3}$ what is a half-subtractor? write its truth table?

Ans:- The half subtractor is a combinational circuit which is used to perform subtraction of two bits.

 → It has two inputs, A (minuend) and B (subtrahend) and two outputs D (Difference) & Bout (Borrow out).




@ Logic Symbol

Inputs		Outputs	
A	B	D	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Truth table

$$D = A \oplus B$$

$$Bout = \bar{A}B$$

 


Logic Diagram

④ Difference between Serial and parallel Address?

Ans:-

Serial Address	parallel Address
① It is slower	① It is faster
② only one bit can add at a time	② All the bits can be added simultaneously
③ only one full address is required irrespective of number of bits	③ Number of full address required is equal to number of bits
④ Economical	④ Costly

⑤ Design 8:1 MUX by using 2:1 MUX?

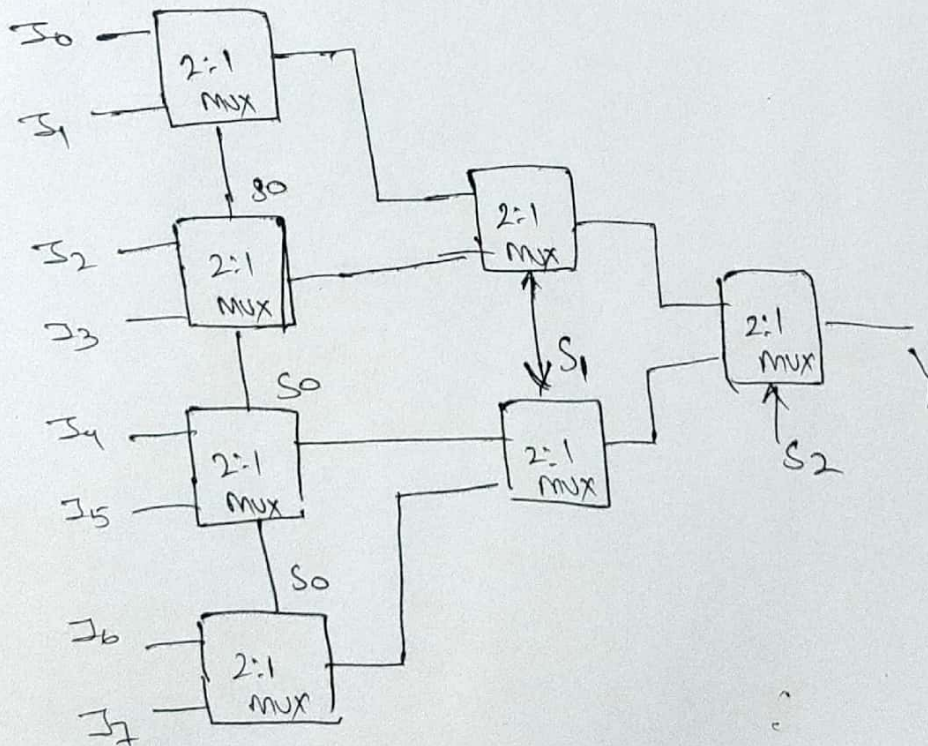

$$\frac{8}{2} = 4 \rightarrow 1^{st} \text{ stage}$$

$$\frac{4}{2} = 2 \rightarrow 2^{nd} \text{ stage}$$

$$\frac{2}{2} = 1 \rightarrow 3^{rd} \text{ stage}$$

Q List the applications of Encoders & decoders.

Ans Applications:

Encoder: These are used to convert one form of data into binary. These are used as

- ① Decimal to Binary converters (BCD)
- ② Octal to Binary converters
- ③ Hexadecimal to Binary converters
- ④ used to drive 7 segment displays.

Decoder: These are used to convert binary data into other form. These are used as

- ① BCD to decimal conversion
- ② Binary to octal conversion
- ③ Hexadecimal to Binary conversion
- ④ BCD to gray (or) gray to BCD conversion.